
lotguider

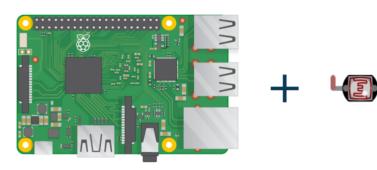

Getting Started Guide for Internet of Things

Posts



Interfacing Light Dependent Resistor LDR in Raspberry Pi

© September 10, 2017

lotguider

6 Comments

Learn interfacing Light Dependent Resistor LDR in Raspberry Pi. We will learn how LDR works. LDR is a type of resistor whose resistance varies according to the surrounding light. Resistance will increase with the increase in light intensity. LDR also known as Photoresistor, are available in 5mm, 7mm, 10mm, and many other sizes. So, let's start.

Search ...

Sign up for Newsletter

Iotguider's Recent Posts

Arduino Fundamentals
Certification Program

Announced New
Arduino MKR WAN
1310 for LoRa
connectivity


Raspberry Pi 4 Model B: Most powerful Raspberry Pi ever!

Step 1: Required Components

LDR (Light Dependent Resistor) x 1
Breadboard x 1
Raspberry Pi x 1
1µf Capacitor x 1
Jumper Wires

Step 2: Circuit Time

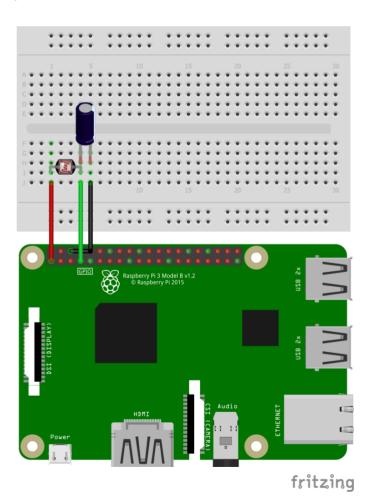Make the circuit as per the given diagram. Connect one leg of LDR to VCC +5v. Now, connect the long leg of the capacitor and another leg of LDR on the same track of breadboard. The ground short leg of the capacitor.



ESP8266 OTA (Over The Air) Update using Arduino IDE

Send HTTP POST Request with ESP8266 WiFi Module

Slack invite

Join lotguider on slack by the following link go.iotguider.in/slack

Step 3: Code Time


This is code for interfacing LDR in Raspberry Pi. First of all, we have to import the LightSensor code for LDR from the gpiozero library. Assign GPIO pin to variable LDR and also pass the GPIO pin number as an argument to the LightSensor method. While loop print's value of LDR.

```
from gpiozero import LightSensor
ldr = LightSensor(4)
while True:
print(ldr.value)

Interfacing_Light_Dependent_Resistor_(LDR)_in_Raspberry_Piview raw
py hosted with by GitHub
```

Step 4: Run code to Raspberry Pi

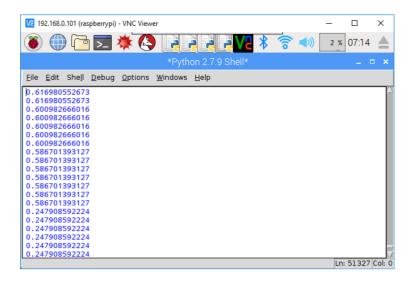Run the Python program in your Raspberry Pi after setting components as per the circuit diagram. The LDR will give resistance to Raspberry Pi and Raspberry Pi. The screenshot of the output is given below.



For running python code in Raspberry Pi, visit: raspberrypi.org/documentation/usage/python/

Love it? Share this among your friends:













Related Posts:

- Interfacing LDR in Arduino
- Interfacing Analog Temperature Sensor KY-013 in Arduino
- What is IoT (Internet of Things)? | Simple...
- What is Arduino Board? | Introduction and brief description
- Using SoftwareSerial in Arduino for Serial Communication
- Hardware Basics of Raspberry Pi 3 Model B

Posted in: Raspberry Pi

Filed under: LDR, Photoresistor, Pi 3, Python, Raspberry

← Ultrasonic Distance Sensor in Raspberry Pi

H-Bridge Motor Driver in Raspberry Pi using python →

6 thoughts on "Interfacing Light Dependent Resistor LDR in Raspberry Pi"



Anders Søndergaard Jensen says:

March 19, 2018 at 2:11 AM

It would be SUPER cool if you corrected the drawing, so the cap is correctly polarized. In the drawing, the cathode is connected to the ldr and the anode is connected to ground, and it should be the other way around, as the text explains.

Reply



lotguider says:

December 14, 2018 at 10:05 PM

Sorry for that. The issue is now changed.

Reply



Hans Koch says:

October 31, 2018 at 1:45 AM

Is it possible to connect several LDR's to Raspberry and maintain Control of each in the Python script?

Reply



Yes it is possible by initializing multiple LDR in code and using it in loop.

Reply



Lukas says:

October 27, 2019 at 6:28 PM

This isnt work well, our metter blink so fast, and sensor didn't catch it at all. Do you have any idea?

Reply



David Sumbler says:

February 8, 2020 at 4:06 PM

This is just what I have been looking for. One query though: in Step 2 you say "Connect one leg of LDR to VCC +5v", but the illustration shows the LDR connected to pin 1, which is 3.3v, rather than one of the 5v pins 2 & 4. Which is correct? I think it probably should be 3.3v, but I don't understand enough to be sure.

Reply

Leave a Reply

Enter your comment here... Copyright © 2021 lotguider